Experiment no. 2

Experiment Name: Designing 2 input CMOS NAND gate using MICROWIND.

Objective: To design CMOS NAND gate and see the performance and output wave shape.
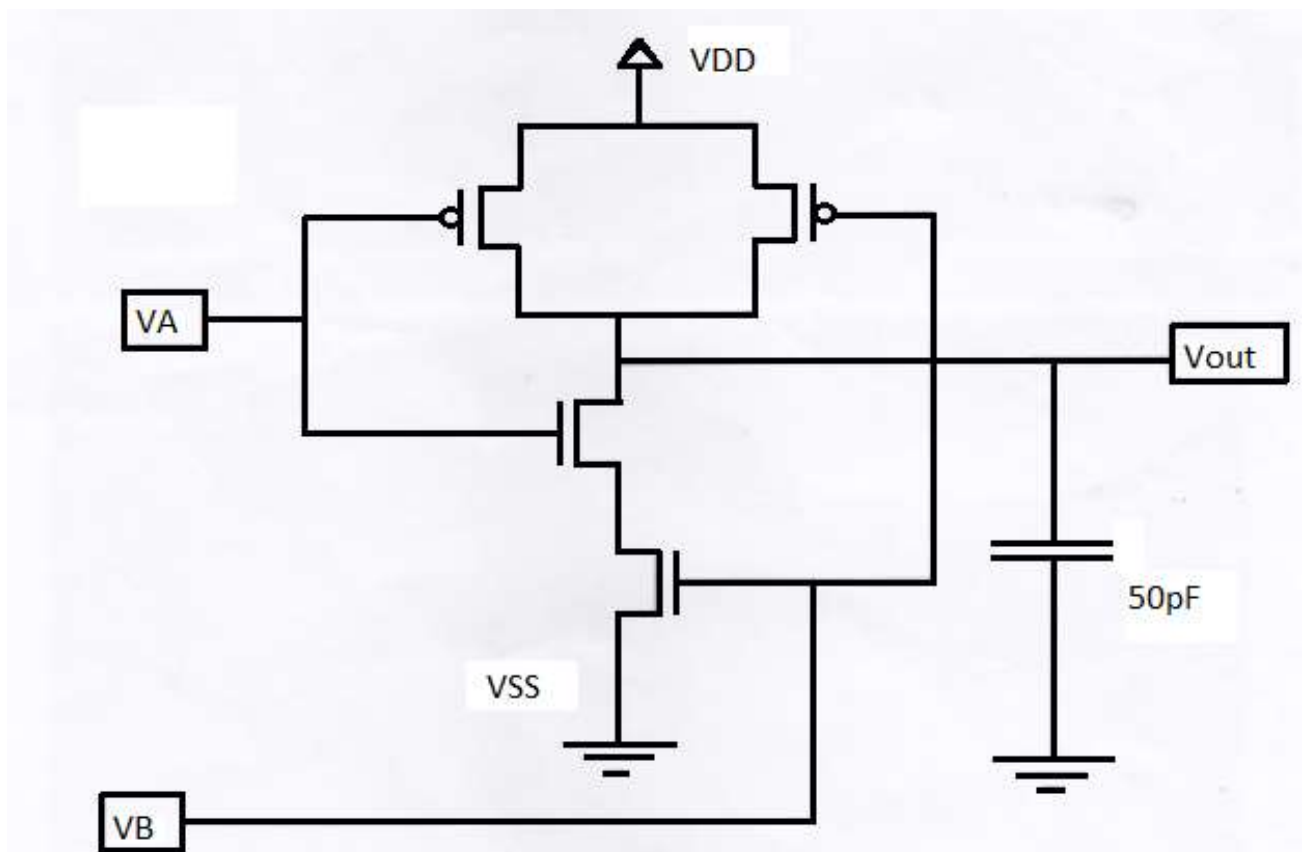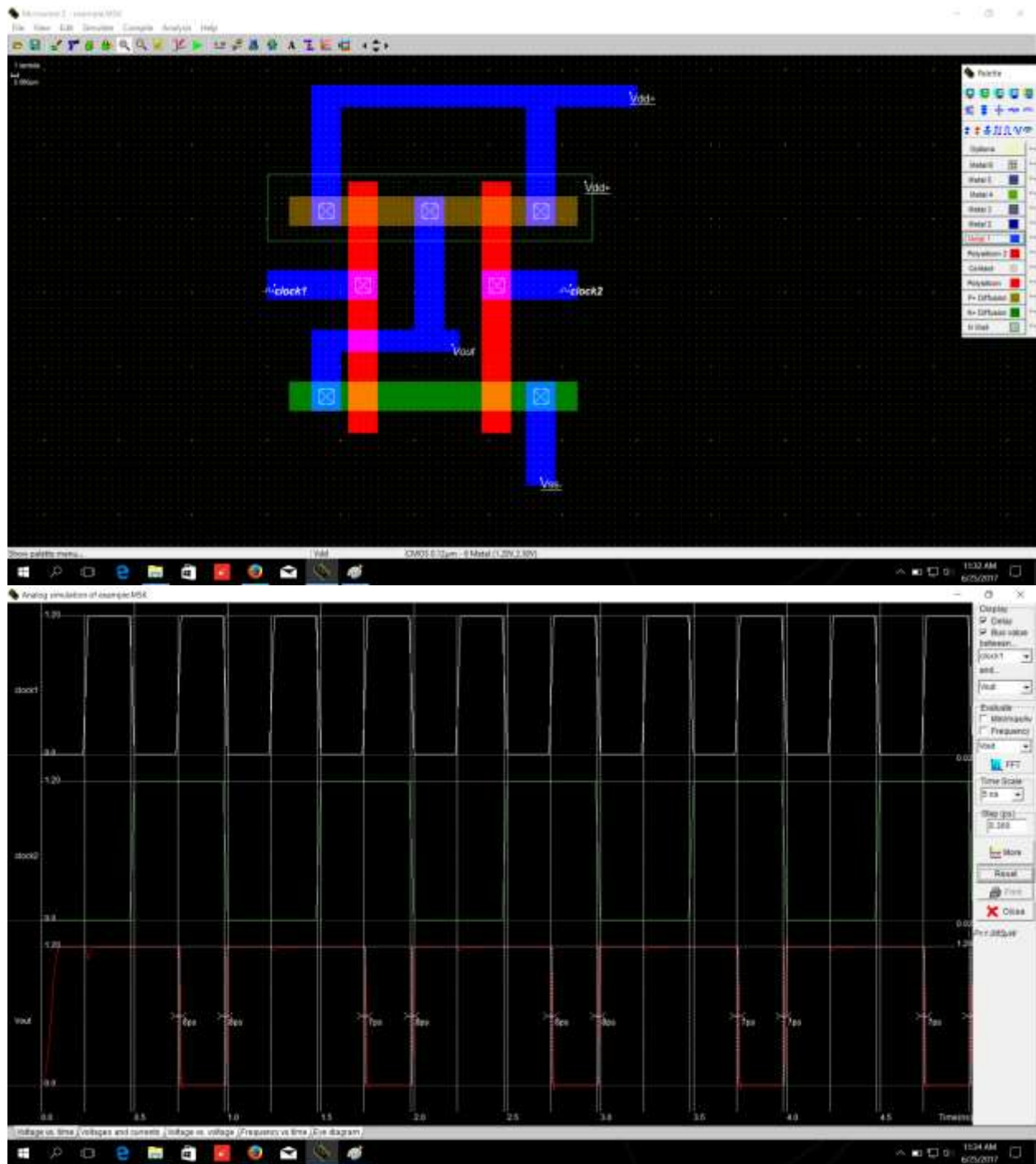
Theory:

Figure 1: CMOS NAND Gate.

Procedure: As mentioned in Lab Manual of Experiment 1.

Question:

1. Design a 3 input CMOS NAND Gate.